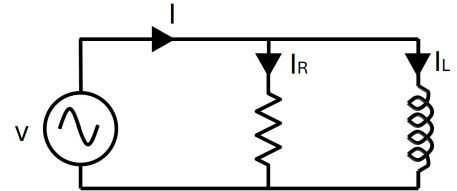





In this topic, we have listed some of the AC Parallel circuit formulas.

**For RL and RC Parallel Circuit:**

**RL Parallel Circuit**



**RC Parallel Circuit**

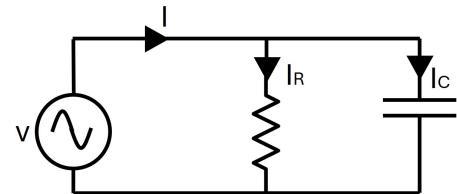

**For RL Parallel and RC Parallel Circuit**

$$I = \sqrt{I_R^2 + I_L^2}$$

$$I = \sqrt{I_R^2 + I_C^2}$$

**For RL:**

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \frac{1}{X_L^2}}$$

**For RC :**

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \frac{1}{X_C^2}}$$

**For RL:**

$$\tan\{\phi\} = \frac{V_L}{V_R} = \frac{X_L}{R}$$

**For RC:**

$$\tan\{\phi\} = \frac{V_C}{V_R} = \frac{X_C}{R}$$

I = Total line current

$I_R$  = Current flow through the resistance

$I_L$  = Current flow through the inductance

$I_C$  = Current flow through the capacitance

Z = Impedance

R = Resistance


$X_L$  = Inductive Reactance

$X_C$  = Capacitive Reactance

Circuit current I lags behind the applied voltage V by  $\phi$

**For parallel RLC Circuit:**

**RLC Parallel Circuit**

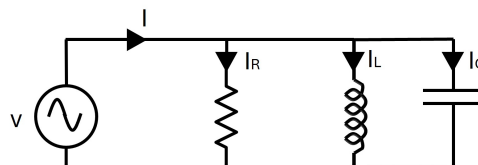

I = Total line current

$I_R$  = Current flow through the resistance

$I_L$  = Current flow through the inductance

$I_C$  = Current flow through the capacitance

**For RLC Parallel:**

$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$



**For RLC Parallel:**

$$Y = \sqrt{G^2 + (B_L - B_C)^2}$$

$$Z = \frac{1}{\sqrt{G^2 + B^2}}$$

Where,

$$Y = \frac{1}{Z}$$

$$G = \frac{1}{R}$$

$$B_L = \frac{1}{\omega L}$$

$$B_C = \omega C$$

Y = Admittance

G = Conductance

B<sub>L</sub> = Inductive Susceptance

B<sub>C</sub> = Capacitive Susceptance

B = Net Susceptance = B<sub>L</sub> - B<sub>C</sub>

Y = Admittance

G = Conductance

B = Net Susceptance = B<sub>L</sub> - B<sub>C</sub>

$$\cos \phi = \frac{G}{Y}$$

$$\tan \phi = \frac{B}{G}$$

**For RLC Parallel Resonance:**

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

f<sub>r</sub> = Resonance frequency

L = Inductance

C = Capacitance

$$\omega_r = \frac{1}{\sqrt{LC}}$$